

Name: Manoj Shrestha

Group: CE -

Roll: 53

Year/sem: III / II



# Assignment - 1

1. In an alarm system of bank, three sensors are implemented and the alarm is triggered when at least two sensors detect the change. Assuming sensors to output digital values, design a combinational logic circuit for alarm system.

→ solution,

The truth table is:

A	B	C	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


using K-map,

A \ BC	00	01	11	10
0		1	1	
1			1	1

$$y = A'C + AB$$



The circuit diagram is,

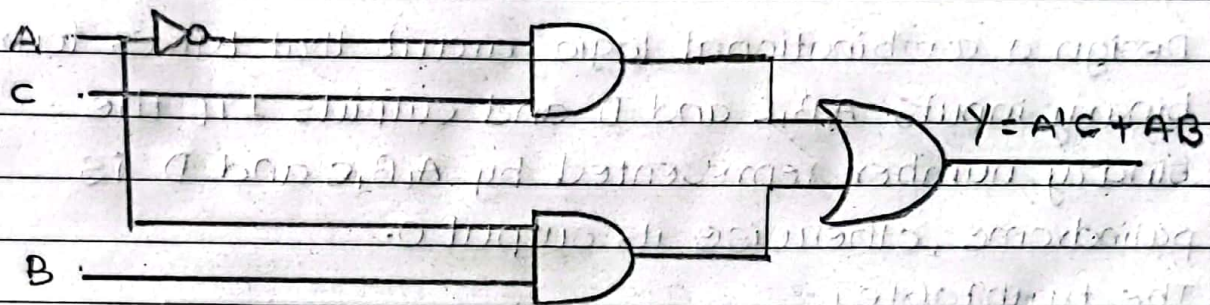

2. Design a combinational logic circuit that takes two binary inputs, A and B, and outputs 1 when the binary number represented by A is greater than the binary number represented by B, otherwise it outputs 0.

→ solution.


The truth table is:

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	0

$$Y = AB'$$



The circuit diagram is,

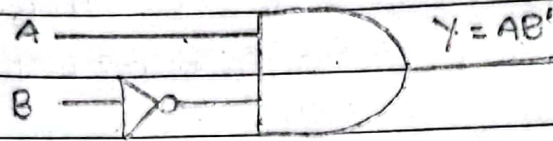

3. Design a combinational logic circuit that takes four binary inputs A, B, C and D and outputs 1 if the binary number represented by A, B, C and D is palindrome, otherwise its output 0.

→ The truth table is:

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1




$$Y = A'B'C'D' + A'BCD' + AB'C'D + ABCD$$

Using K-map

AB \ CD	00	01	11	10
00	1		1	
01				1
11				
10		1		

$$\begin{aligned} Y &= A'B'C'D' + A'BCD' + AB'C'D + ABCD \\ &= A'D'(B'C' + BC) + AD(B'D + BC) \\ &= (B'C' + BC)(A'D' + AD) \\ &= (\overline{B \oplus C})(\overline{A \oplus D}) \end{aligned}$$

The circuit diagram is,

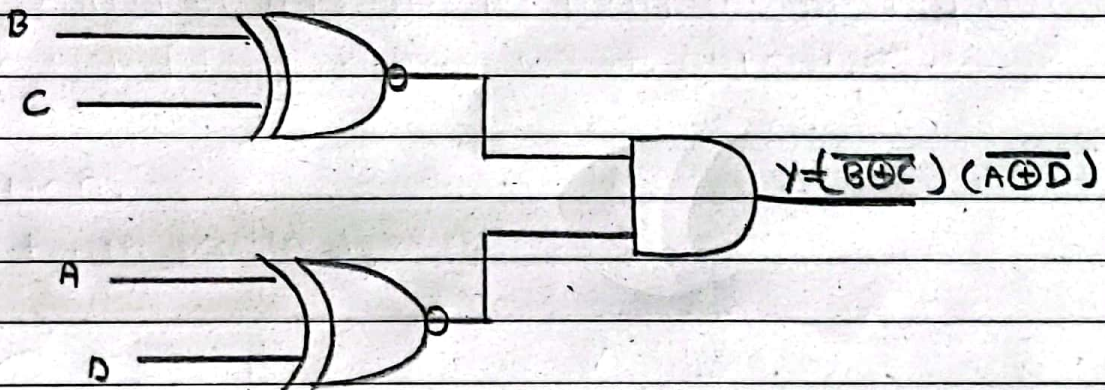



4. Design a combinational logic circuit that takes three binary inputs, A, B, and C and outputs 1 if the binary number represented by A, B, and C is a multiple of 3, otherwise it outputs 0.

→ The truth table is,


SN	A	B	C	Y
1	0	0	0	1
2	0	0	1	0
3	0	1	0	0
4	0	1	1	1
5	1	0	0	0
6	1	0	1	0
7	1	1	0	1
8	1	1	1	0

A \ BC	00	01	11	10
0	1		1	
1				1

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

The circuit diagram is,



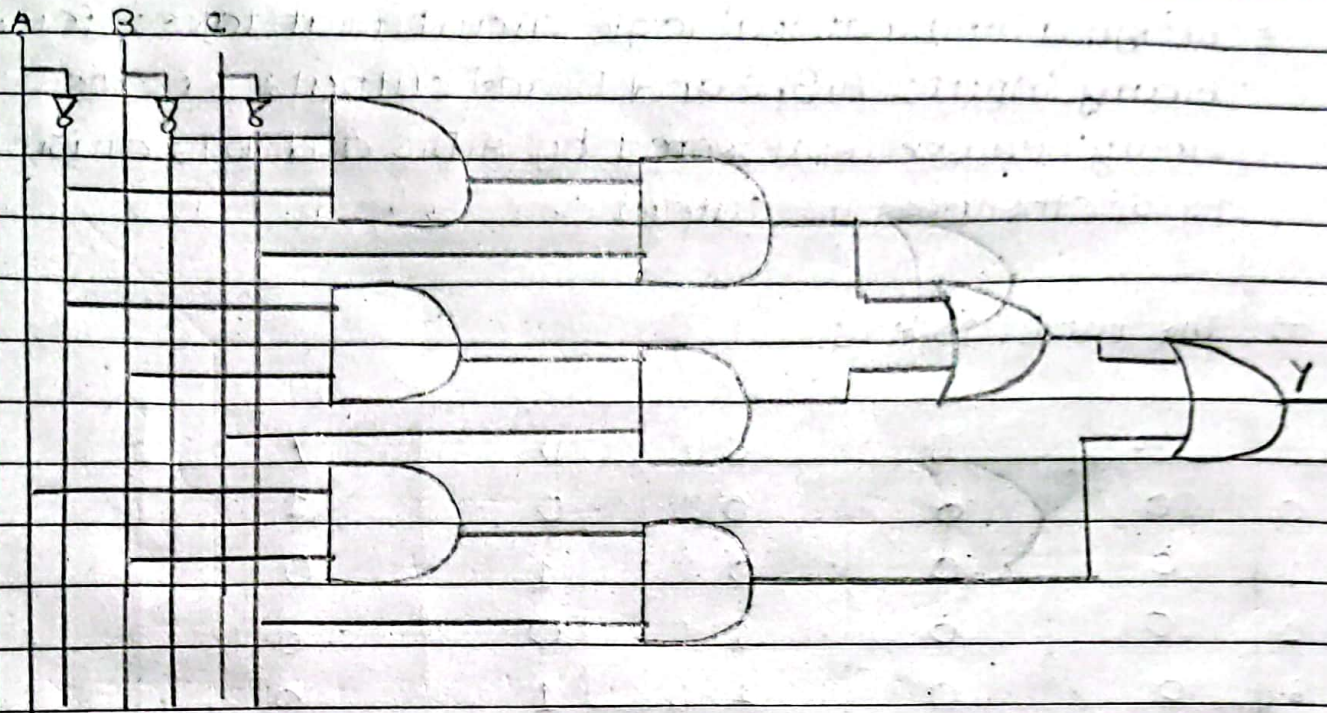



5. Design a combinational logic circuit that takes four binary inputs A, B, C and D and outputs 1 if the binary number represented by A, B, C and D is divisible by 5, otherwise its output 0.

→ The truth table is.


S.N.	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	1



AB \ CD	00	01	11	10
00	1			
01		1		
11			1	
10				1

$$\begin{aligned}
 Y &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}C\bar{D} + ABCD \\
 &= \bar{A}\bar{C}(\bar{B}\bar{D} + BD) + AC(\bar{B}\bar{D} + BD) \\
 &= (\bar{B}\bar{D} + BD)(\bar{A}\bar{C} + AC) \\
 &= (\bar{B} \oplus D)(A \oplus C)
 \end{aligned}$$

The circuit diagram is.

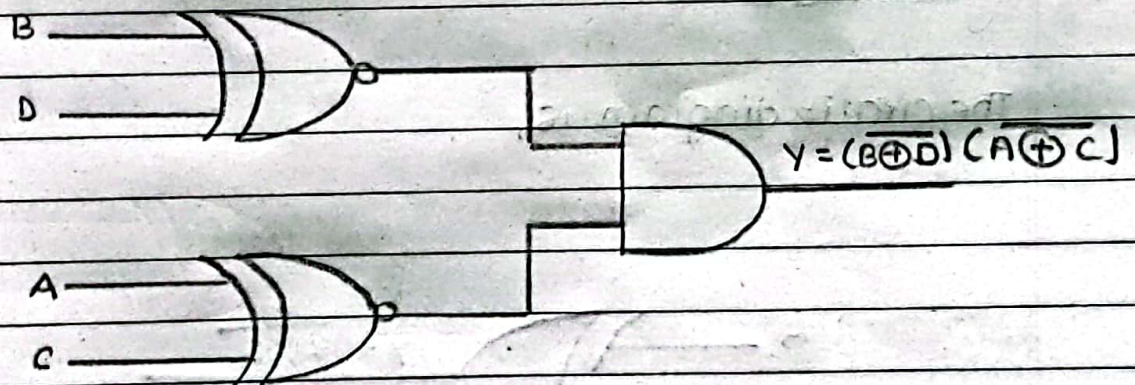



6. Design a combinational logic circuit that takes two binary inputs A, B, C and D and outputs 1 when the binary number represented by A is equal to the binary number represented by B, otherwise its outputs 0.

→ The truth table is:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$Y = A'B' + AB$$

$$= \overline{A \oplus B}$$

The circuit diagram is,

